

Mammal Tracking Project - Current Meter Board Pins Used

Emery Newlon

Primary Processor


The primary processor of the project is a Freescale Kinetis L class microcontroller. The Freescale Freedom board used for this project uses a KL25 version of this processor. In the connection diagrams that follow the color silver indicates an empty hole, black indicates a pin without a connection to it, while other colors indicate the wire color or component connected to the pin.

Freedom Board Pins Used

The Current Meter Board (CMB) is powered by the USB connection through the OpenSDA port. It is connected to an external resistance network board that provides signal taps used to determine the current passing from a current source to its destination. The analog reference is smoothed by capacitor C_R and resistor R_R . The connections to the Current Meter Board are as follows:

- | | |
|--------------------------|-------------------|
| 1. Data In (Optional) | J1-1 to J1-15 odd |
| 2. Data Out (Optional) | Sampling J2-1 |
| 3. AREF Capacitor Low | GND J2-14 |
| 4. AREF Capacitor High | AREF J2-16 |
| AREF Resistor Low | |
| 5. CMB Power (Optional) | P3V3 J9-08 |
| 6. AREF Resistor High | P3V3 J9-04 |
| 7. Resistor Board Ground | GND J9-12 |
| 8. Resistor Board V+ | PTE20 J10-01 |
| 9. Resistor Board V- | PTE21 J10-03 |

$C_R = 1000 \mu F$, $R_R = 1000 \Omega$

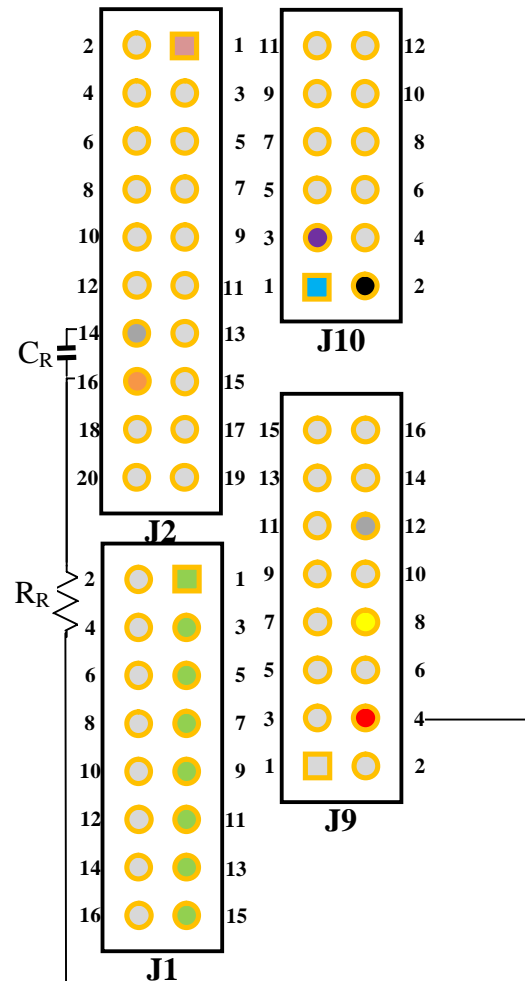

The Resistor Board is used to implement the resistor network and the pins needed to connect it to the Source, Destination, and Current Meter Board. The current through the R_0 resistor is measured by determining the difference between V_+ and V_- assuming that the resistances of R_1 to R_4 are much higher than that of R_0 .

$$V_+ = V_{in} \times R_3 / (R_1 + R_3) \quad \rightarrow \quad V_{in} = V_+ \times (R_1 + R_3) / R_3$$

$$V_- = V_{out} \times R_4 / (R_2 + R_4) \quad \rightarrow \quad V_{out} = V_- \times (R_2 + R_4) / R_4$$

$$I_{out} = (V_{in} - V_{out}) / R_0 \quad \rightarrow$$

$$I_{out} = [V_+ \times (R_1 + R_3) / R_3 - V_- \times (R_2 + R_4) / R_4] / R_0$$

Resistor R_0 is a 1Ω resistor. Resistor R_4 is calibrated by connecting the same voltage source, V_{cal} , across both V_{in} and V_{out} , then adjusting R_4 until V_+ and V_- have the same values. This results in:

$$V_+ = V_{cal} \times R_3 / (R_1 + R_3)$$



&

$$V_- = V_{cal} \times R_4 / (R_2 + R_4)$$

$$V_{cal} \times R_3 / (R_1 + R_3) = V_{cal} \times R_4 / (R_2 + R_4) \quad \rightarrow \quad R_3 / (R_1 + R_3) = R_4 / (R_2 + R_4)$$

$$(R_1 + R_3) / R_3 = (R_2 + R_4) / R_4 \quad \rightarrow \quad I_{out} = [(V_+ - V_-) \times (R_1 + R_3) / R_3] / R_0$$

1. Source Ground	GND	RB-10
2. Source Vcc	Vin	RB-11
3. CMB V+	V+	RB-09
4. CMB Ground	GND	RB-08
5. CMB V-	V-	RB-05
6. Destination Ground	GND	RB-06
7. Destination Vcc	Vout	RB-01

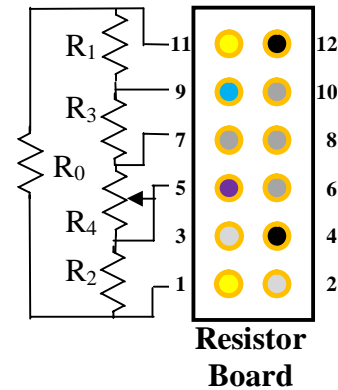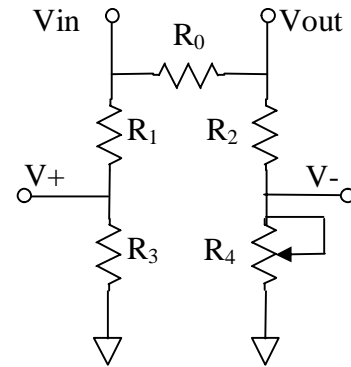

V_+ must be less than A_{REF} . If max V_+ is $(g \times A_{REF})$:

$$g \times A_{REF} / V_{in} = R_3 / (R_1 + R_3)$$

$$g \times A_{REF} / V_{in} = 1 / (R_1 / R_3 + 1)$$

$$R_1 / R_3 = 1 / (g \times A_{REF} / V_{in}) - 1$$

$$R_1 = R_3 \times [1 / (g \times A_{REF} / V_{in}) - 1]$$

where g is a constant such as 0.9.

$R_4 = 2 \times R_3$ to allow for it to be adjusted.

Calibrate using calibration cable:

Connect blue to the red.

Apply power (3.3v) between red and black.

Adjust R_2 until voltage between yellow and green is 0.

Measure V_{cal} between red and black.

Measure V_{+cal} between yellow and black.

Disconnect red and black from power and ground.

Disconnect blue from red.

Set power to 0.3v or less.

Connect red to power, blue to ammeter, and ammeter to ground.

Measure I_{cal} through ammeter and V_{Lcal} between red and blue.

Calculate calibration factor for this Resistor Board:

$$CF = (V_{cal} / V_{+cal}) / (V_{Lcal} / I_{cal})$$

$$I_{out} = (V_{+} - V_{-}) \times CF$$

